

DVD A01 REPORT


Nishchal Gaur

2022330

Problem Statement

Design an Inverter, simulate with eldo ,Size it to achieve same rising and falling delays..


Schematic


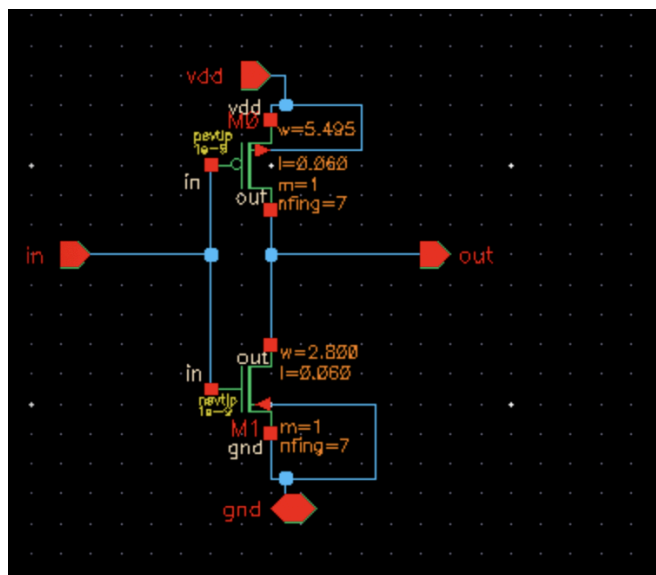


Rise and Fall Delays

TPLH	=	2.3453E-11
TPHL	=	2.4594E-11
TFALL	=	2.3217E-11
TRISE	=	2.3611E-11
DELAY	=	2.4023E-11

Eldo Waveforms

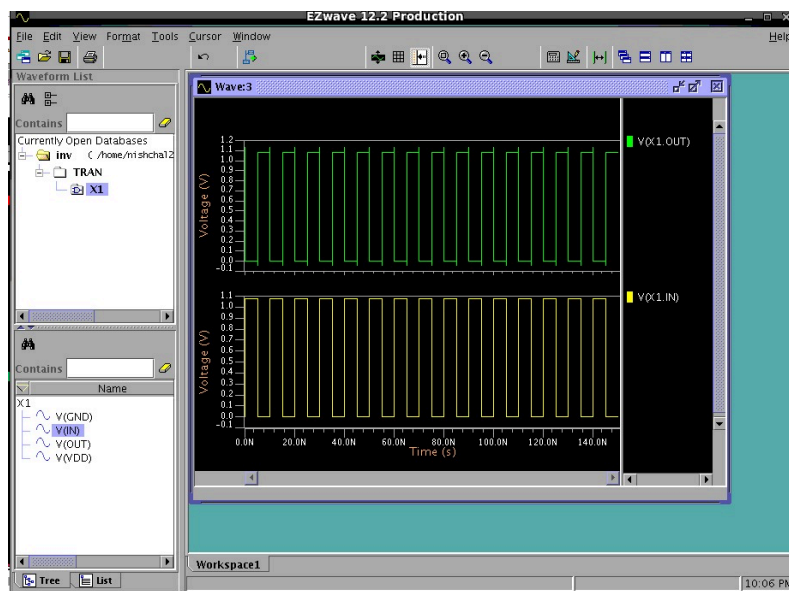

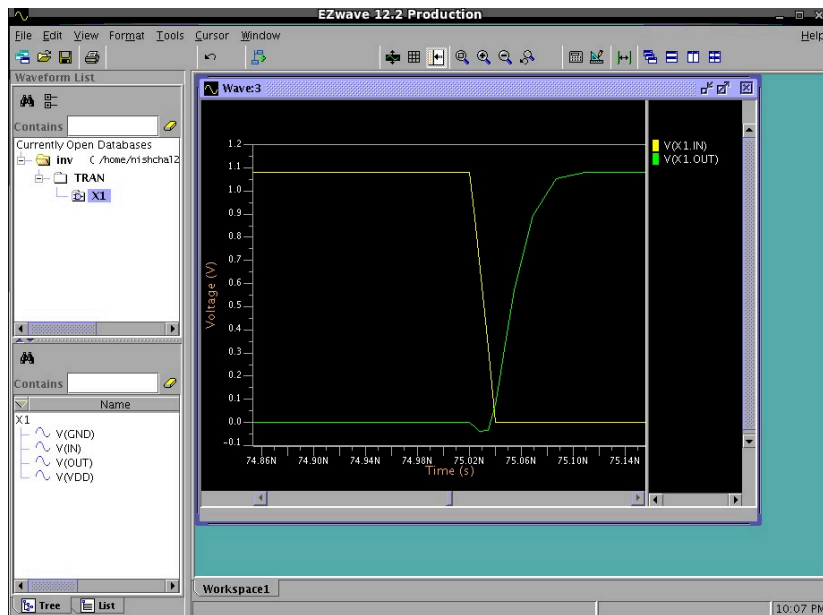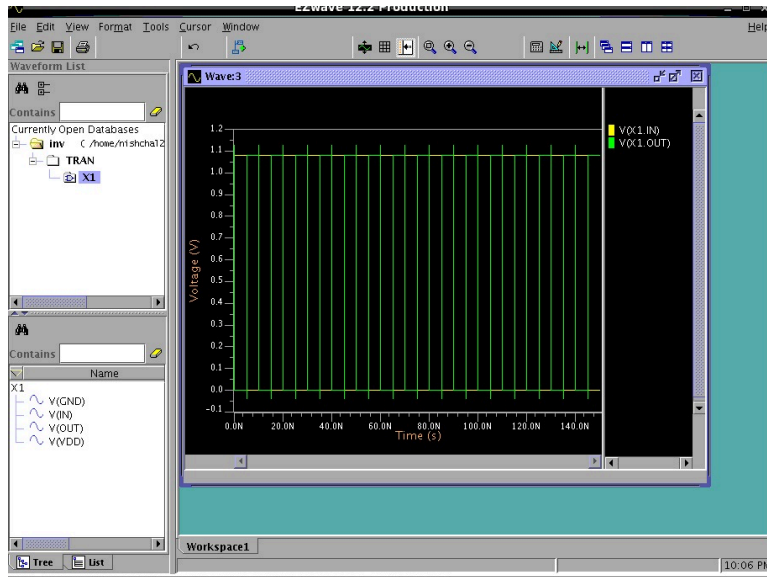

Spectre Waveform (step input is given)

